

May 2, 2014 • no comments

Electrical Salinometer Working Principle

韌 Share

璣 Tweet


敲 Pin

鑄 Mail

Working Principle of Salinometer

The electrical supply to the salinometer must be DC. The potentiometer is provided to give a fixed standard calibration voltage so that no errors to voltage differences exist.

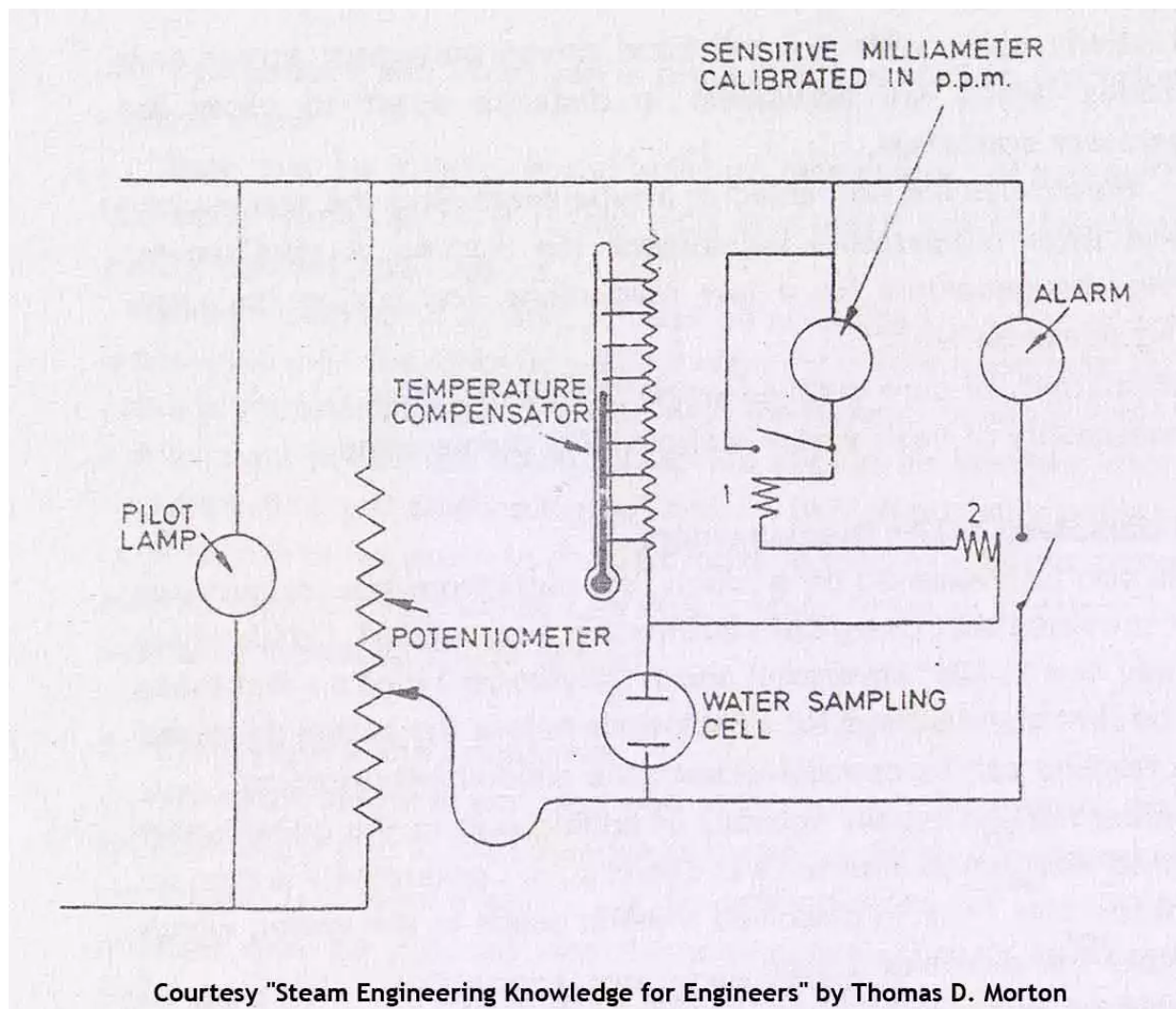Pure water is non-conducting so that current flow is an indication of impurities, i.e. the greater the current the greater the impurity in the water. Figure below shows a salinometer usually found with a freshwater generator.




When the impurity content exceeds a fixed value the current is sufficient to operate the relay 2 so giving visual or audible warning by closing the circuit. Continued operation at increased current would cause Relay 1 to short circuit the meter and so protect it.

Water temperature increases conductivity so that temperature compensation is required. A temperature compensating thermometer is a shunt across the meter. Temperature increase causes a rise of mercury level and a cutting out of resistance which allows more current through the shunt and less through the meter. The correct calibration current through the meter is fixed; current variations due to temperature are shunted.

References

“Steam Engineering Knowledge for Engineers” by Thomas D. Morton

Related Posts

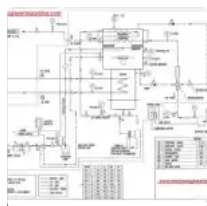

April 25, 2015

[Operation of Freshwater Generator with Jacket Cooling Water](#)



April 24, 2015

[Shell and Tube Freshwater Generator](#)




May 2, 2014

[Fresh water Generator on Ships](#)




May 27, 2014

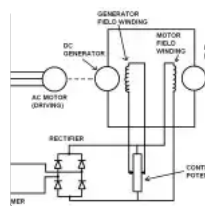[Parallel Operation Procedure for Marine Diesel Generators in Ships](#)




May 2, 2014

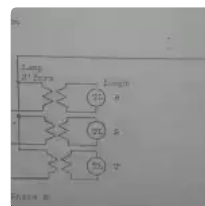[Ward Leonard Speed Control System for a DC Motor](#)




May 29, 2014

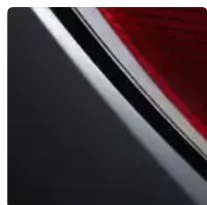[Earth Fault Indicator Circuit in Ships](#)




February 6, 2016

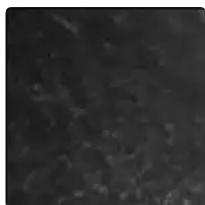[Troubleshooting Alarm Monitoring and Control System on ships](#)



May 25, 2014

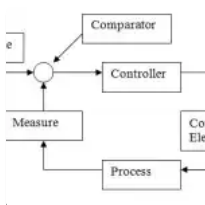[Diesel Generator Control Procedure on Installation in Ships](#)



May 6, 2014

[Basic Temperature Control System](#)



May 24, 2014

[Operation of Circuit Breakers on Main Switch Board in Ships](#)

Previous Post

[額 DC Generator Working Principle And Parts](#)

Next Post

[Non-Destructive Tests On Metals 類](#)

Leave a Reply

Name*

E-Mail*

Website

Publish

[⤴ Back to top](#)

Mobile

Desktop